

# Operational Amplifiers

Op-amp for short

Pat Arnott 360 ATMS

## 'History'

1928 Harold Black invents feedback amplifier.

1947 Ragazzini first uses the term Operational Amplifier in print.


Bardeen, Brattain, and Shockley of Bell LABS discover the transistor effect.

< Transfer of Resistance

1953 First commercially available vacuum tube op-amp.

1958 Jack Kilby of Texas Instruments invents the integrated circuit.

1963 Bob Widlar of Fairchild designs the first monolithic IC op-amp  $\Rightarrow$  Single chip.

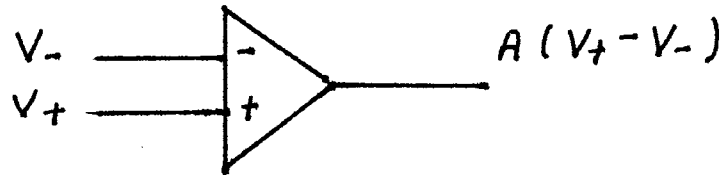
Basic Op-Amp

Inputs:  
 $V_+$  &  $V_-$

Output:  
 $A(V_+ - V_-)$   
↑  
Huge

$$A = \text{Gain} \approx 100,000$$

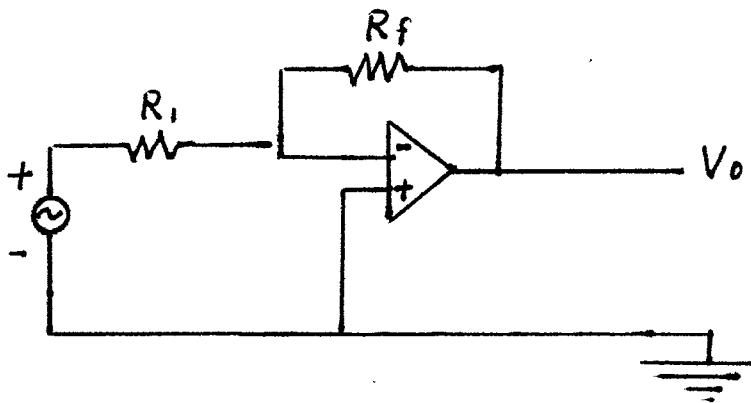
Need to clobber the gain a bit to reduce the instability:



Feedback some of the output to the input to reduce instability.
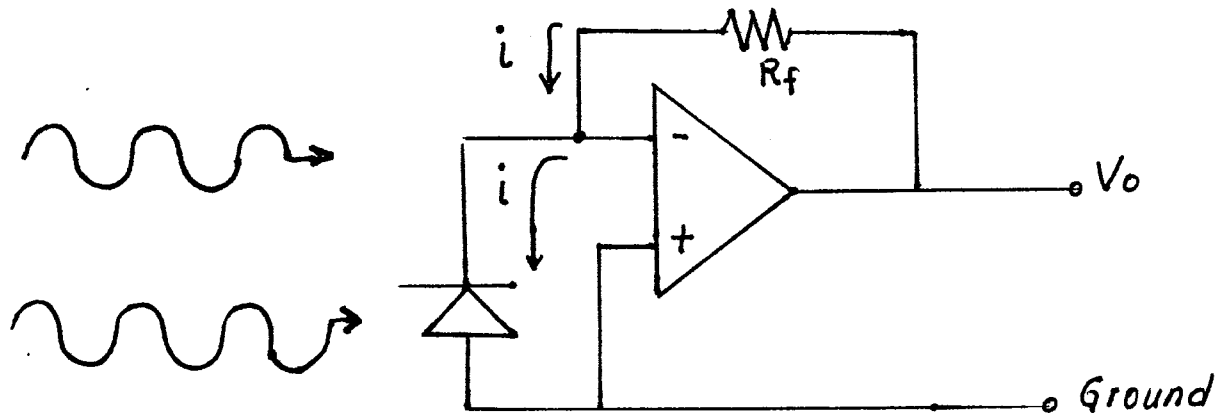
## Transimpedance Amplifier

(Turn the current produced by an LED with light shining on it, into a measurable voltage).



Analyze this circuit using the Op-amp golden rules

- 1)  $V_o$  feedback keeps the voltage the same at the - and + terminals of the Op-amp.
- 2) The - and + terminals have extremely high input impedance: No current flows into either terminal.

Analysis:  $i$  = current generated by the LED when light shines on it.


From rule 2,  $i$  is the current flowing through  $R_f$  also.

From rule 1, - and + terminals are both at ground voltage.

Ohms Law gives  $V_o = iR_f$  or  $i = 1\mu\text{a}$ ,  $R_f = 1\text{M}\Omega$   
 $V_o = 1\text{ volt}$

## Simple Circuits

### 1) Inverting Amplifier:

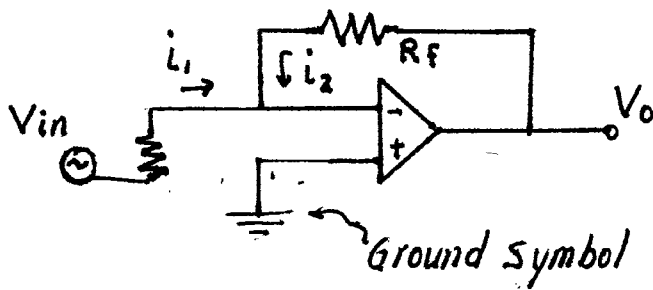


Output is measured from  $V_o$  to ground.  
Goal: Amplify  $V_{in}$  by turning it into  $V_{out}$

$V_o$  is the output voltage  
 $V_{in}$  is the input voltage

- Sign inversion  $\Rightarrow$   
Gain =  $R_f / R_i$

Rule 2:  $i_1 + i_2 = 0$

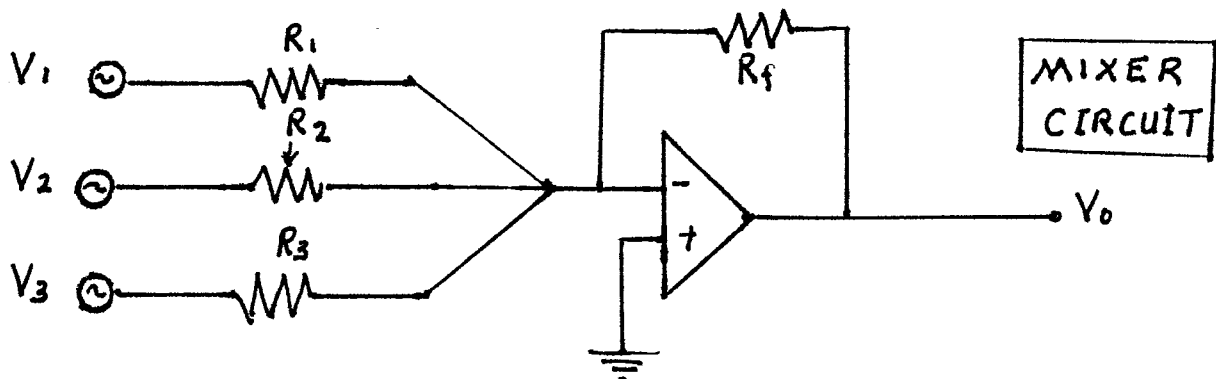Rule 1 & Ohm's Law:  $\frac{V_{in}}{R_i} + \frac{V_o}{R_f} = 0$ , So  $\boxed{\frac{V_o}{V_{in}} = -\frac{R_f}{R_i}}$



$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_o}{R_f} = 0$  With  $R_1 = R_2 = R_3$

$\boxed{V_o = -(V_1 + V_2 + V_3) \left( \frac{R_f}{R_i} \right)}$

Gain =  $R_f / R_i$

Input voltages are summed & amplified